 


1) Design a 4 bit combinational circuit decrementer using 4 FA's




$$A-1 = A + 2'S \text{ Complement of } 1 \\ = A + 1111.$$

2) An arithmetic circuit has 2 selection variables S1 and S0. The arithmetic operation available in the unit are listed below. Determine the circuit that must be incorporated with the full adder in each stage of the arithmetic circuit.

S1 S0	Ci=0	Ci=1
0 0	$F = A+B$	$F = A+B+1$
0 1	$F = A$	$F = A+1$
1 0	$F = \overline{B}$	$F = \overline{B} + 1$
1 1	$F = A + \overline{B}$	$F = A + \overline{B} + 1$

Solution:

 Let the input to the full adder circuit can be X_i & Y_i



$$X_i = A_i S_1 + A_i S_0$$

$$Y_i = B_i \overline{S_1} \overline{S_0} + \overline{B_i} S_1$$

S1 S0 Ai Bi	Xi Yi	Function
0 0 0 0	0 0	Xi= Ai Yi= Bi
0 0 0 1	0 1	
0 0 1 0	1 0	
0 0 1 1	1 1	
0 1 0 0	0 0	Xi=Ai Yi=0
0 1 0 1	0 0	
0 1 1 0	1 0	
0 1 1 1	1 0	
1 0 0 0	0 1	Xi=0 Yi= \overline{Bi}
1 0 0 1	0 0	
1 0 1 0	0 1	
1 0 1 1	0 0	
1 1 0 0	0 1	Xi=Ai Yi=Bi
1 1 0 0	0 0	
1 1 0 0	1 1	
1 1 0 0	1 0	

- 3) Design an arithmetic circuit with one selection variable S and two data inputs A & B. The circuit generates the following 4 arithmetic operations in conjunction with the input carry Cin. Draw the logic diagram for the first two stages.

S	Cin=0	Cin=1
0	D=A+B (add)	D=A+1(increment)
1	D=A-1(decrement)	D=A+ \overline{B} +1(sub)

S	Cin	X	Y
0	0	A	B (A+B)
0	1	A	0 (A+1)
1	0	A	1(A-1)
1	1	A	\overline{B} (A-B)

