

# Unsigned Multiplication


# Multiplication of Unsigned Numbers

$$\begin{array}{r}
 \begin{array}{cccc}
 & 1 & 1 & 0 & 1 \\
 \times & 1 & 0 & 1 & 1 \\
 \hline
 & 1 & 1 & 0 & 1 \\
 & 1 & 1 & 0 & 1 \\
 & 0 & 0 & 0 & 0 \\
 1 & 1 & 0 & 1 & \\
 \hline
 1 & 0 & 0 & 0 & 1 & 1 & 1 & 1
 \end{array}
 \end{array}$$

(13) Multiplicand M  
(11) Multiplier Q  
(143) Product P

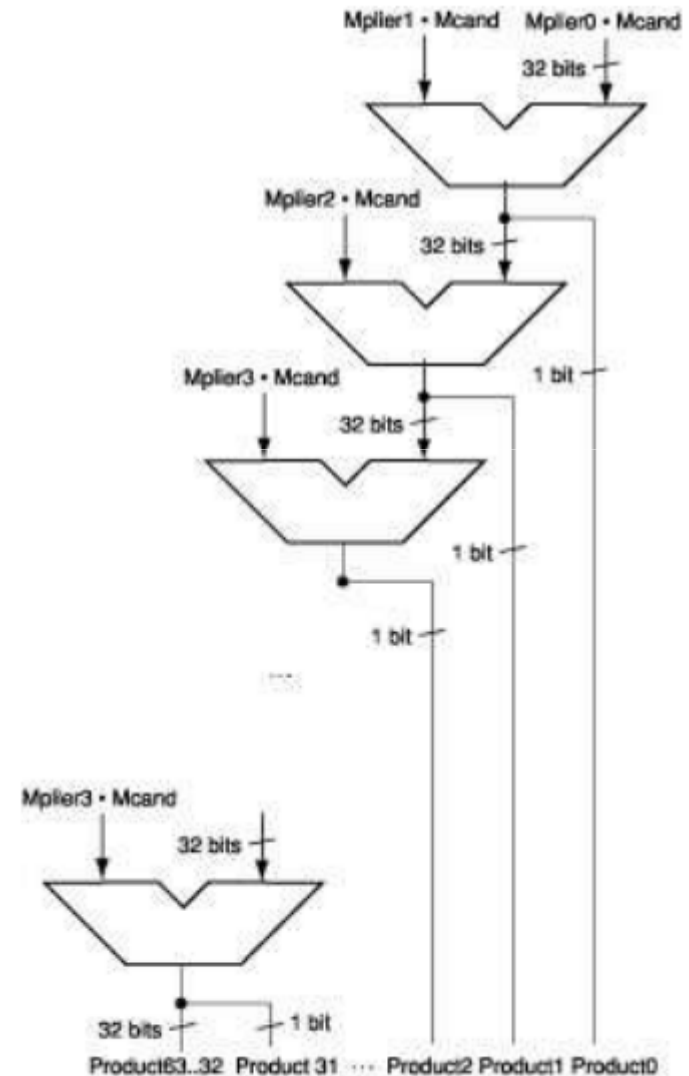(a) Manual multiplication algorithm


Multiplication of two fixed-point binary numbers in signed magnitude representations is done by a process of successive **shift and add operations**



# Multiplication of Unsigned Numbers


- The process consists of looking at successive bits of the multiplier, LSB first.
- If the multiplier bit is a 1 → multiplicand is copied down  
0 → zeroes are copied down.
- The number copied down in successive lines are shifted one position to the left from the previous number finally the numbers are added and their sum forms a product.
- Sign of the product is determined from the signs of the multiplicand and multiplier.
  - If they are alike the sign of the product is positive.
  - If they are unlike the sign of the product is negative

# Array Multiplier

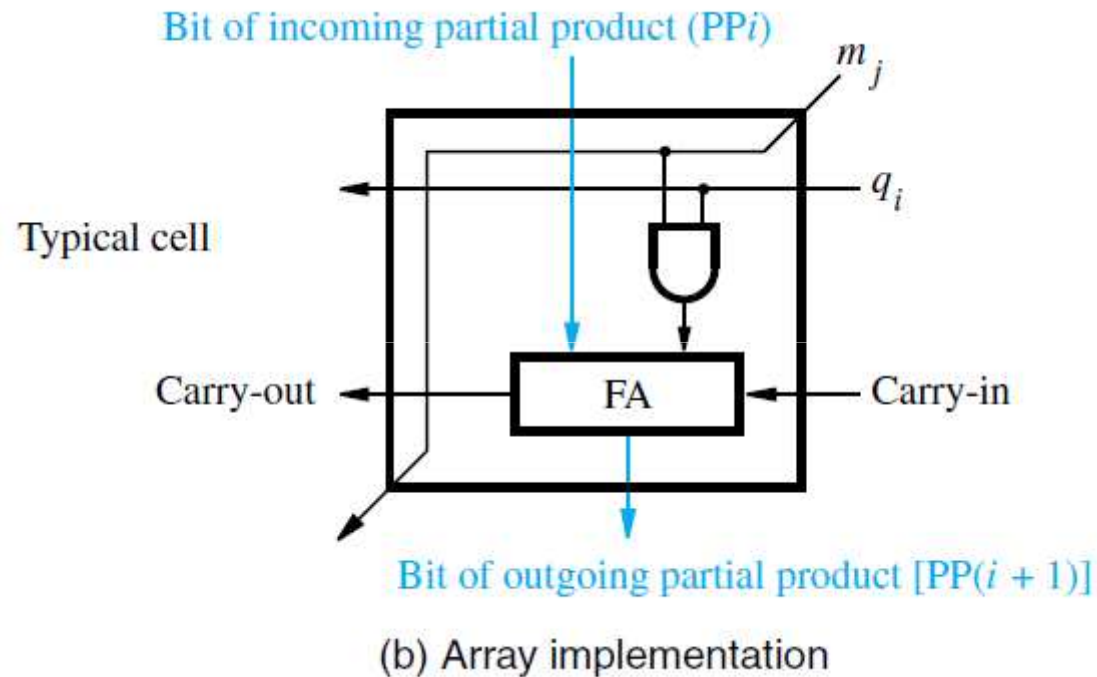


Combinational logic & Array Implementation

# Array Multiplier

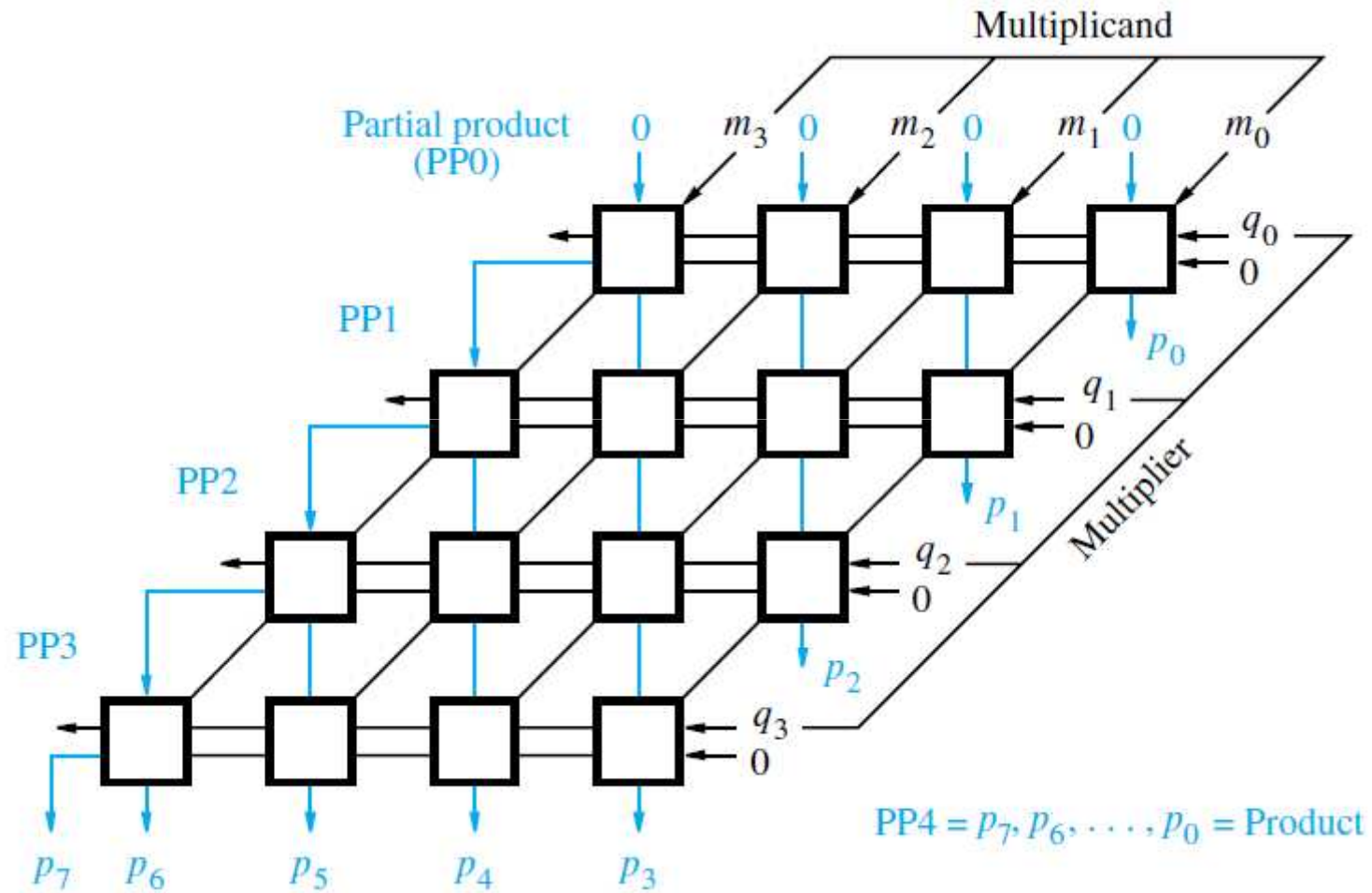

Combinational logic & Array Implementation


# Sequential Circuit Multiplier

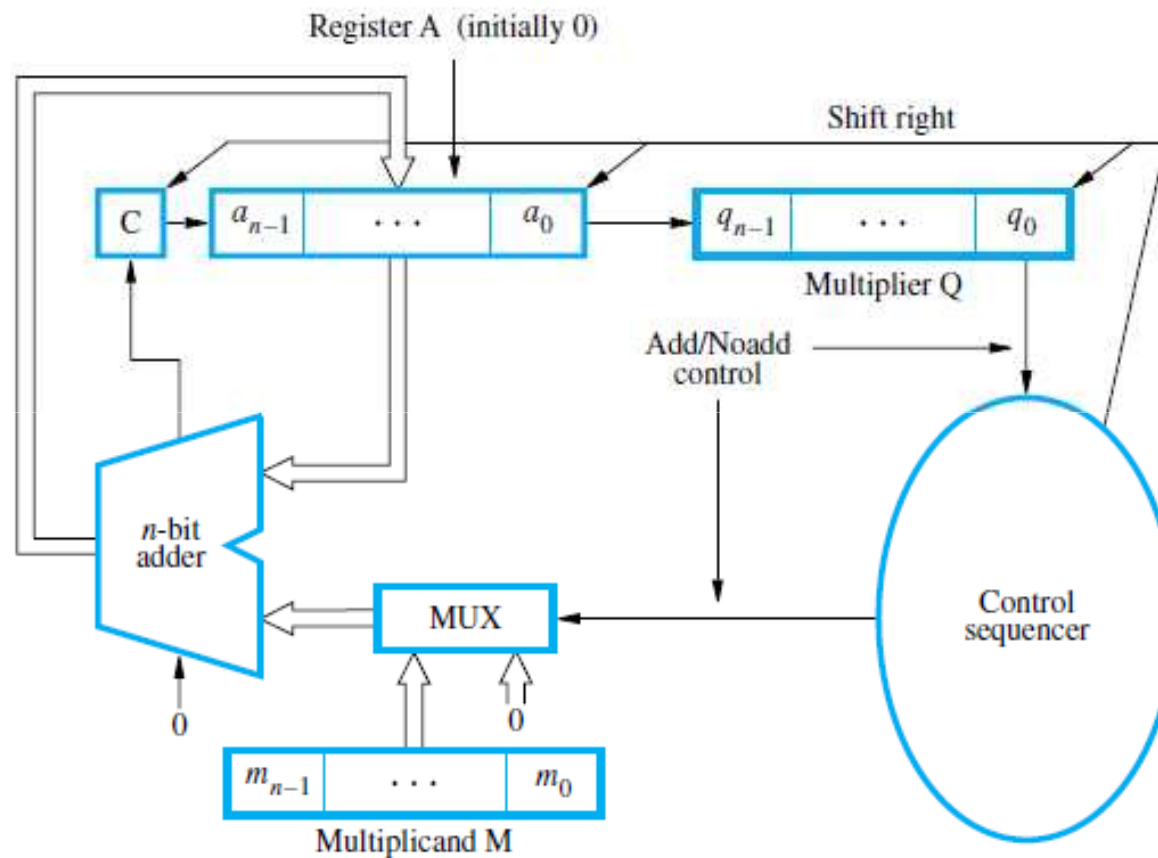

(a) Register configuration

Final Version


# Sequential Circuit Multiplier

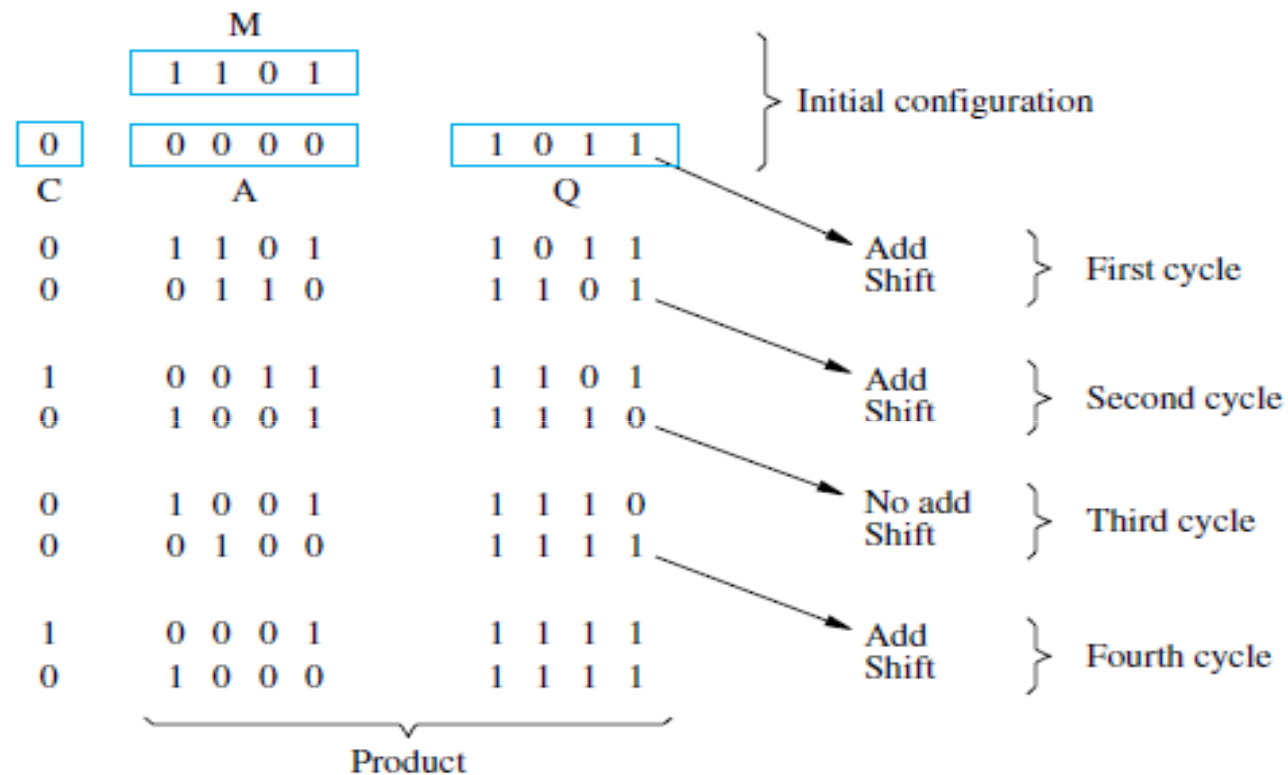

(b) Multiplication example


Sequential circuit binary multiplier.

# Multiplication Hardware First version

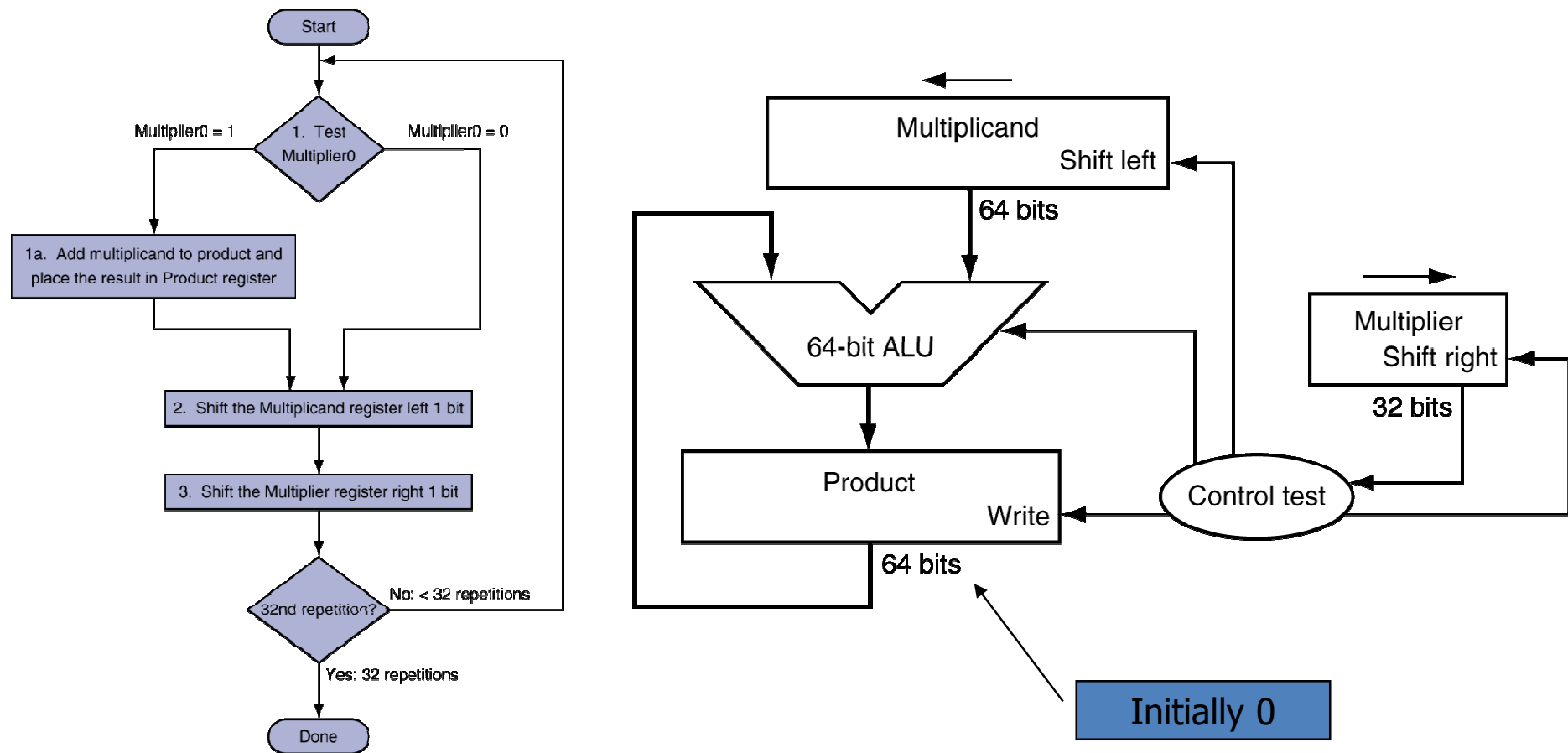




# Second Version

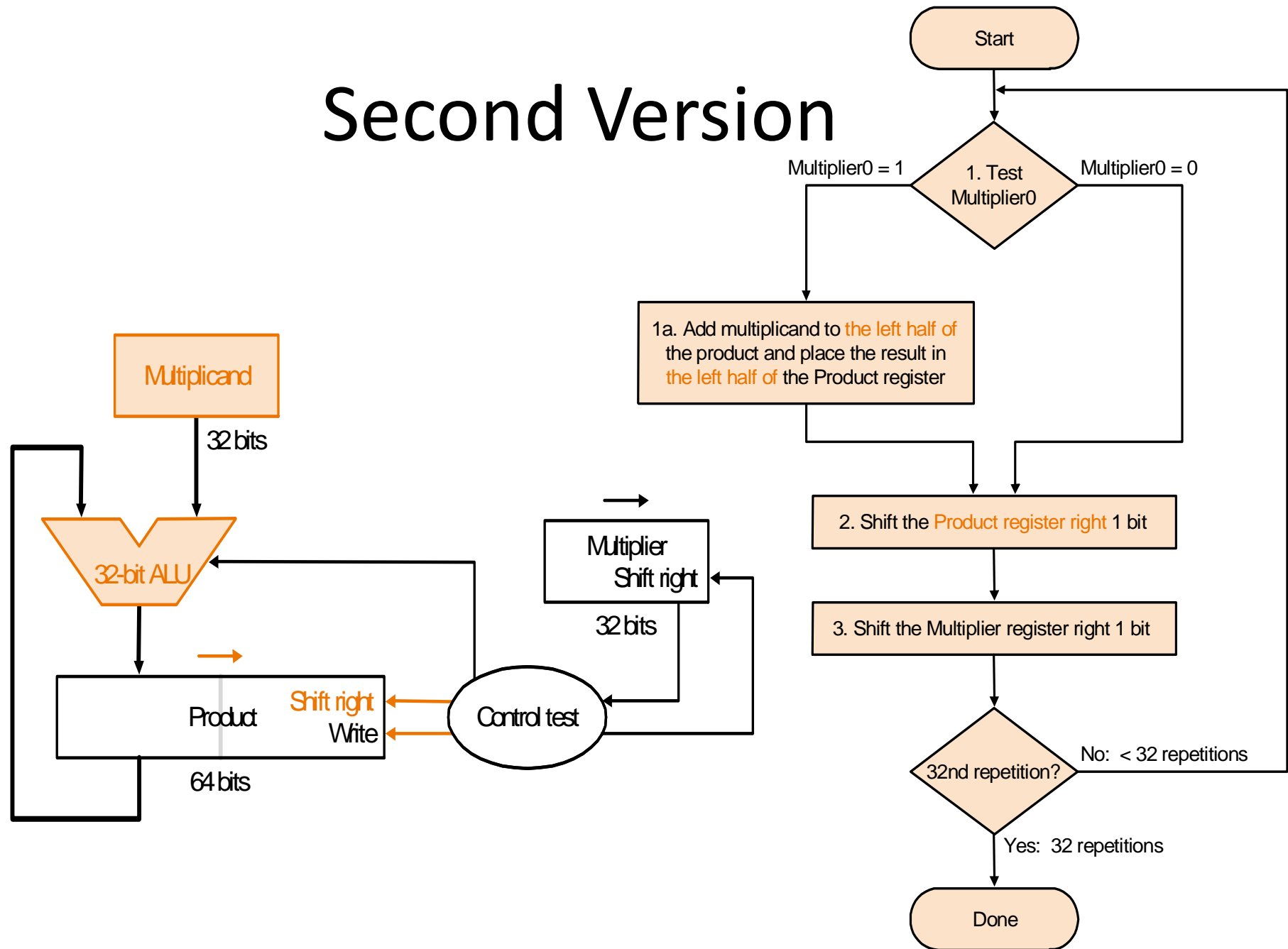

# Final Version

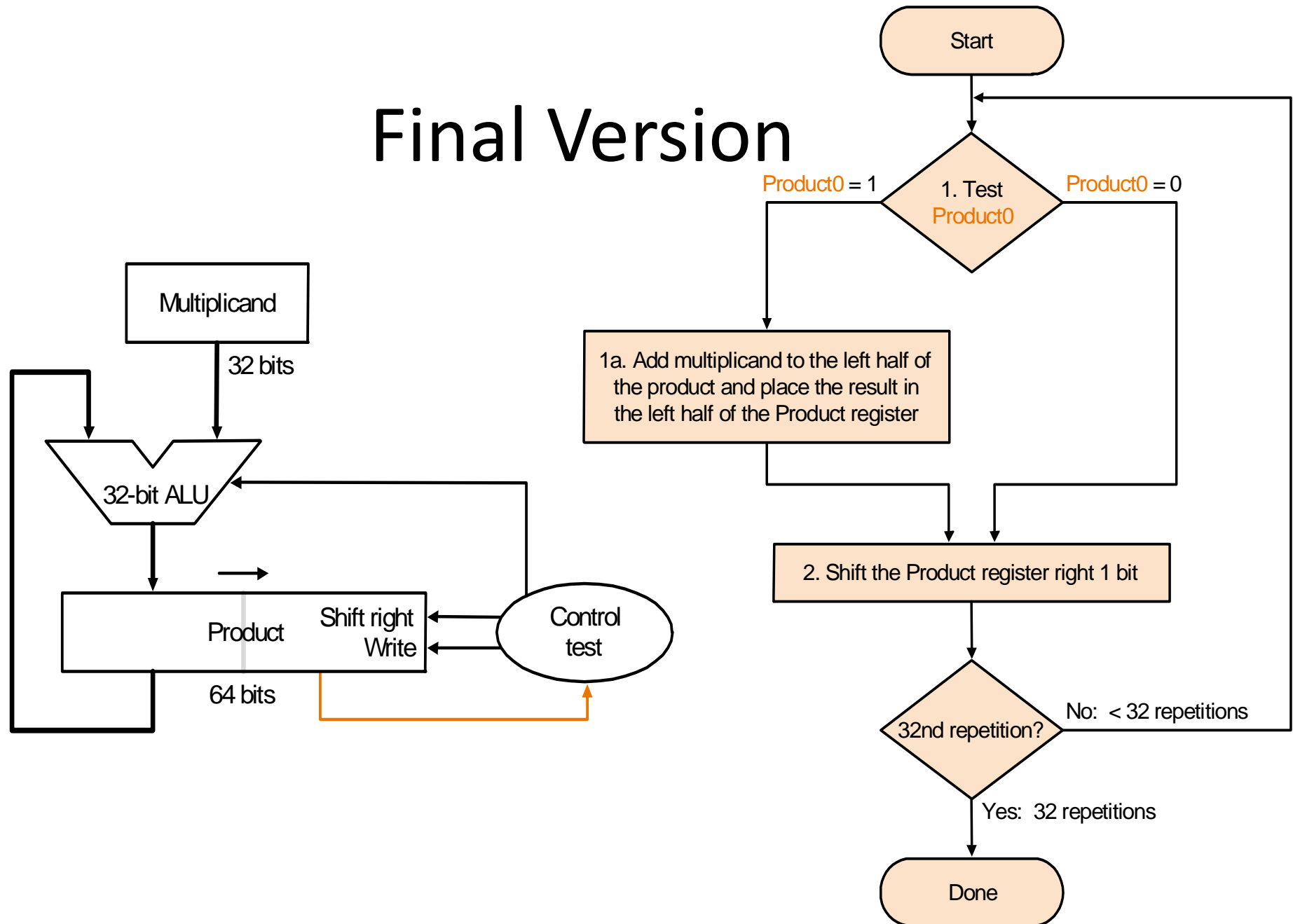

# Signed Multiplication

# Signed Multiplication

- Considering 2's-complement signed operands, what will happen to  $(-13) \times (+11)$  if following the same method of unsigned multiplication?

						1	0	0	1	1	(-13)	
					×	0	1	0	1	1	(+11)	
						<hr/>						
					1	1	0	0	1	1		
				1	1	0	0	1	1			
			1	1	0	0	0	0				
		1	1	0	0	1	1					
	1	1	0	0	0	0						
	<hr/>											
	1	1	0	1	1	1	0	0	0	1	(-143)	

Sign extension is shown in blue

Sign extension of negative multiplicand.

# Signed Multiplication

- For a negative multiplier, a straightforward solution is to form the 2's-complement of both the multiplier and the multiplicand and proceed as in the case of a positive multiplier.
- This is possible because complementation of both operands does not change the value or the sign of the product.
- A technique that works equally well for both negative and positive multipliers – Booth algorithm.

# Booth Algorithm

- Consider in a multiplication, the multiplier is positive 0011110, how many appropriately shifted versions of the multiplicand are added in a standard procedure?

$$\begin{array}{r}
 \begin{array}{cccccccc}
 & & & & & & & 0 & 1 & 0 & 1 & 1 & 0 & 1 \\
 & & & & & & & 0 & 0 & +1 & +1 & +1 & +1 & 0 \\
 \hline
 & & & & & & & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 & & & & & 0 & 1 & 0 & 1 & 1 & 0 & 1 & & \\
 & & & 0 & 1 & 0 & 1 & 1 & 0 & 1 & & & & \\
 & & 0 & 1 & 0 & 1 & 1 & 0 & 1 & & & & & \\
 & 0 & 1 & 0 & 1 & 1 & 0 & 1 & & & & & & \\
 & & 0 & 0 & 0 & 0 & 0 & 0 & 0 & & & & & \\
 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & & & & & & \\
 \hline
 0 & 0 & 0 & 1 & 0 & 1 & 0 & 1 & 0 & 0 & 0 & 1 & 1 & 0
 \end{array}
 \end{array}$$

Normal multiplication schemes

# Booth Algorithm

- Handles both positive and negative multipliers uniformly
- it achieves some efficiency in the number of additions required when the multiplier has a few large blocks of 1s.

# Booth Algorithm

- Since  $0011110 = 0100000 - 0000010$ , if we use the expression to the right, what will happen?

$$\begin{array}{r}
 0100000 \quad (32) \\
 - 0000010 \quad (2) \\
 \hline
 0011110 \quad (30)
 \end{array}$$

								0	1	0	1	1	0	1
								0	+1	0	0	0	-1	0
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	1	1	1	1	1	0	1	0	0	1	1	← 2's complement of the multiplicand
0	0	0	0	0	0	0	0	0	0	0	0	0		
0	0	0	0	0	0	0	0	0	0	0	0			
0	0	0	0	0	0	0	0	0	0	0				
0	0	0	1	0	1	1	0	1						
0	0	0	0	0	0	0	0							
0	0	0	1	0	1	0	1	0	0	0	1	1	0	

Booth multiplication schemes.



# Booth Algorithm


Multiplier		Version of multiplicand selected by bit $i$
Bit $i$	Bit $i - 1$	
0	0	$0 \times M$
0	1	$+ 1 \times M$
1	0	$- 1 \times M$
1	1	$0 \times M$

Booth multiplier recoding table.

The Booth technique for recoding multipliers is summarized in Figure

# Booth Algorithm

- In general, in the Booth scheme, -1 times the shifted multiplicand is selected when moving from 0 to 1, and +1 times the shifted multiplicand is selected when moving from 1 to 0, as the multiplier is scanned from right to left.


0	0	1	0	1	1	0	0	1	1	1	0	1	0	1	1	0	0
																	
0	+1	-1	+1	0	-1	0	+1	0	0	-1	+1	-1	+1	0	-1	0	0

Booth recoding of a multiplier.


The transformation *is called skipping over 1s*.

# Booth Algorithm


Worst-case  
multiplier

0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	
																
+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	

Ordinary  
multiplier

1	1	0	0	0	1	0	1	1	0	1	1	1	1	0	0	
																
0	-1	0	0	+1	-1	+1	0	-1	+1	0	0	0	-1	0	0	

Good  
multiplier

0	0	0	0	1	1	1	1	1	0	0	0	0	1	1	1	
																
0	0	0	+1	0	0	0	0	-1	0	0	0	+1	0	0	-1	

Booth recoded multipliers.

# Booth Algorithm: Example


$  \begin{array}{r}  0\ 1\ 1\ 0\ 1 \\  \times 1\ 1\ 0\ 1\ 0 \\  \hline  \end{array}  $	$\Rightarrow$	$  \begin{array}{r}  0\ 1\ 1\ 0\ 1 \\  0\ -1\ +1\ -1\ 0 \\  \hline  \end{array}  $
		$  \begin{array}{r}  0\ 0\ 0\ 0\ 0 \\  1\ 1\ 1\ 1\ 1 \\  0\ 0\ 0\ 0\ 1 \\  1\ 1\ 1\ 0\ 0 \\  0\ 0\ 0\ 0\ 0 \\  \hline  1\ 1\ 1\ 0\ 1\ 1\ 0\ 0\ 1\ 0  \end{array}  $
		$(-78)$

Booth multiplication with a negative multiplier.

# Fast Multiplication
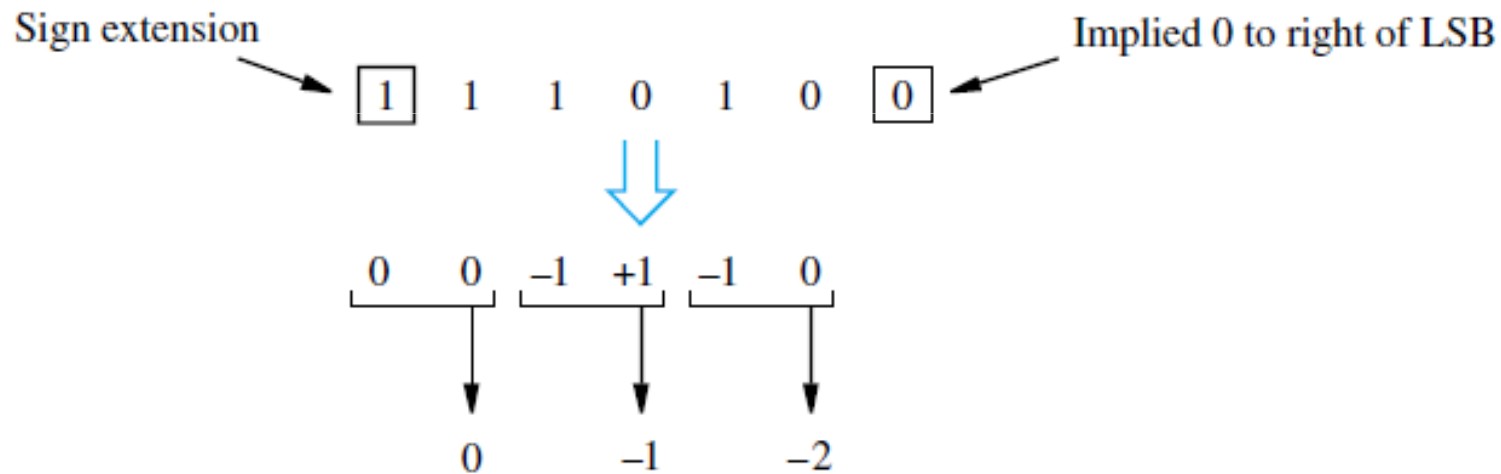
# Bit-Pair Recoding of Multipliers

- Derived directly from the Booth algorithm
- Group the Booth-recoded multiplier bits in pairs



Example of bit-pair recoding derived from Booth recoding

# Bit-Pair Recoding of Multipliers

Multiplier bit-pair		Multiplier bit on the right $i - 1$	Multiplicand selected at position $i$
$i + 1$	$i$		
0	0	0	$0 \times M$
0	0	1	$+ 1 \times M$
0	1	0	$+ 1 \times M$
0	1	1	$+ 2 \times M$
1	0	0	$- 2 \times M$
1	0	1	$- 1 \times M$
1	1	0	$- 1 \times M$
1	1	1	$0 \times M$

(b) Table of multiplicand selection decisions

# Bit-Pair Recoding of Multipliers

$$\begin{array}{r} 01101 \text{ (+13)} \\ \times 11010 \text{ (-6)} \\ \hline \end{array}$$

$$\begin{array}{r} 01101 \\ 0-1-2 \\ \hline 1111100110 \\ 11110011 \\ 000000 \\ \hline 1110110010 \end{array}$$

Bit-Pair Recoding


Multiplication requiring only  $n/2$  summands.

$$\begin{array}{r} 01101 \\ 0-1+1-10 \\ \hline 0000000000 \\ 111110011 \\ 00001101 \\ 1110011 \\ 000000 \\ \hline 1110110010 \text{ (-78)} \end{array}$$

Booth




# Carry-Save Addition of Summands

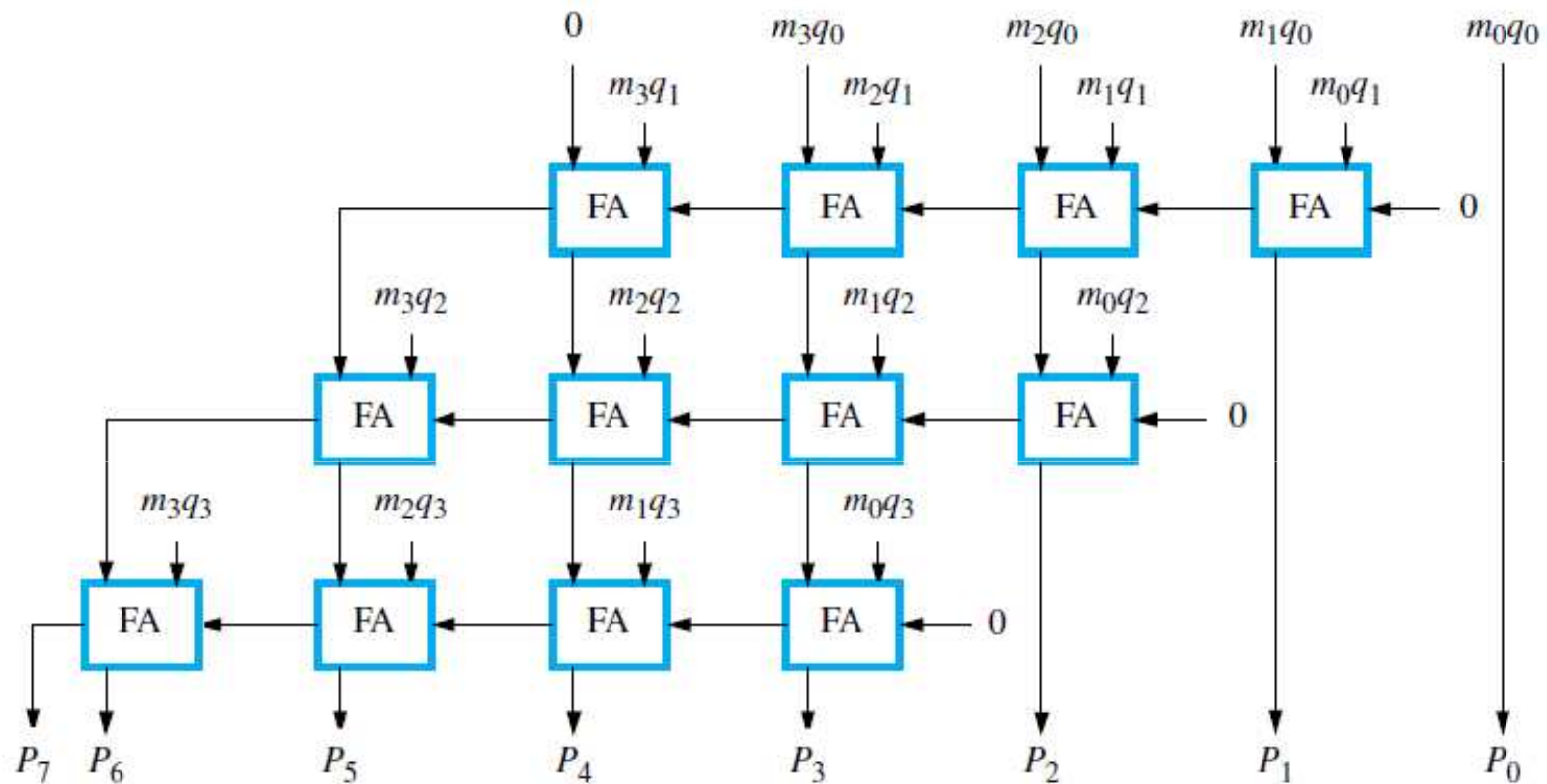

(a) Ripple-carry array

# Carry-Save Addition of Summands

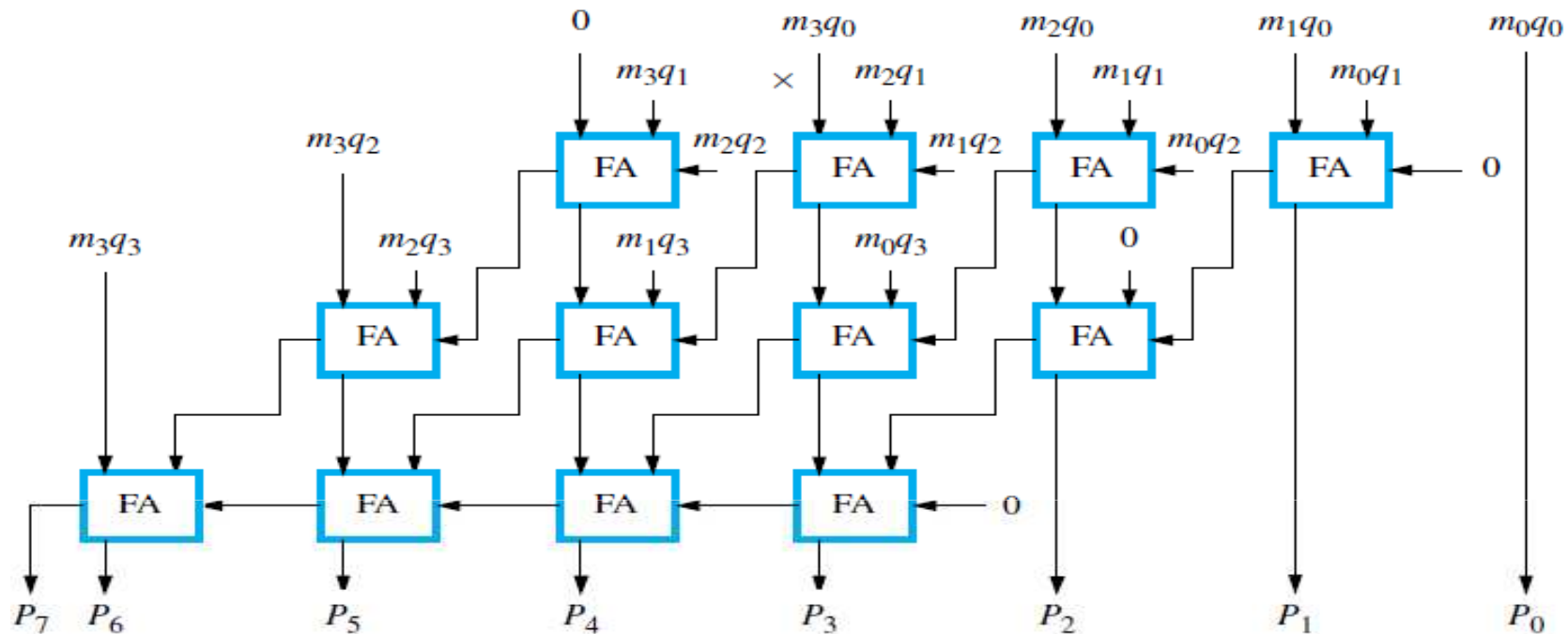

(b) Carry-save array

Ripple-carry and carry-save arrays for a  $4 \times 4$  multiplier.

The delay through the carry-save array is somewhat less than delay through the ripple-carry array. This is because the S and C vector outputs from each row are produced in parallel in one full-adder delay.

# Carry-Save Addition of Summands

- Consider the addition of many summands
  - Group the summands in threes and perform carry-save addition on each of these groups in parallel to generate a set of S and C vectors in one full-adder delay
  - Group all of the S and C vectors into threes, and perform carry-save addition on them, generating a further set of S and C vectors in one more full-adder delay
  - Continue with this process until there are only two vectors remaining
  - They can be added in a RCA or CLA to produce the desired product


# Carry-Save Addition of Summands

						1	0	1	1	0	1	(45)	M
						×	1	1	1	1	1	(63)	Q
<hr/>													
						1	0	1	1	0	1		A
					1	0	1	1	0	1			B
				1	0	1	1	0	1				C
			1	0	1	1	0	1					D
		1	0	1	1	0	1						E
	1	0	1	1	0	1							F
<hr/>													
1	0	1	1	0	0	0	1	0	0	1	1	(2,835)	Product

A multiplication example used to illustrate carry-save addition



# Carry-Save Addition of Summands

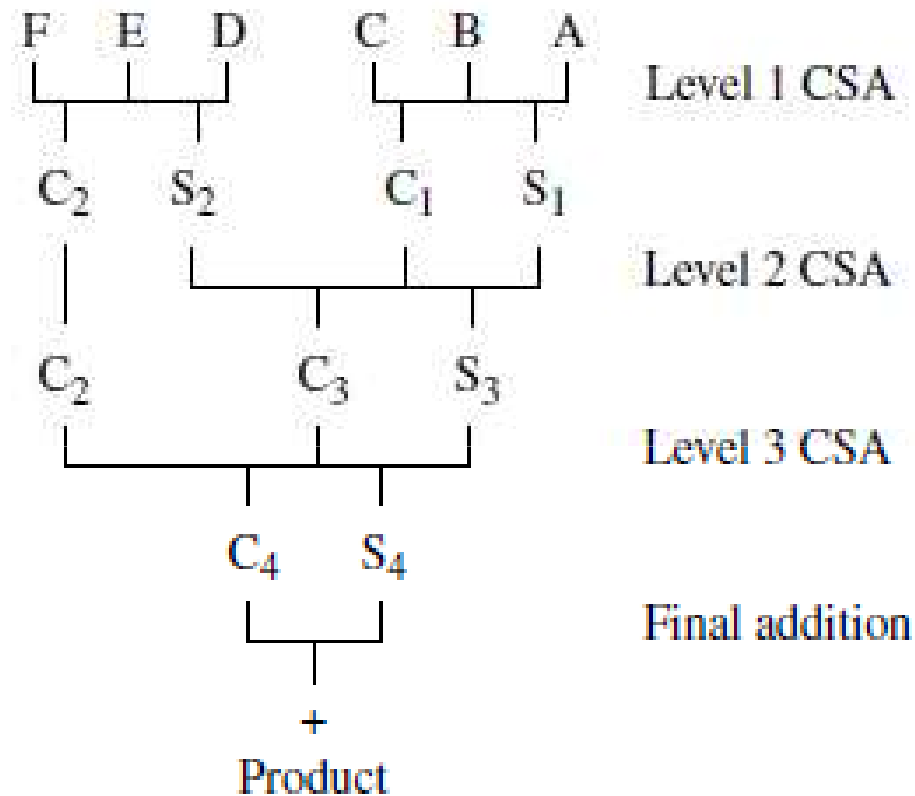

Schematic representation of the carry-save addition operations


# Integer Division

$$\begin{array}{r} 21 \\ 13 \overline{) 274} \\ \underline{26} \\ 14 \\ \underline{13} \\ 1 \end{array}$$

$$\begin{array}{r} 10101 \\ 1101 \overline{) 100010010} \\ \underline{1101} \\ 10000 \\ \underline{1101} \\ 1110 \\ \underline{1101} \\ 1 \end{array}$$

Longhand division examples.

# Restoring Division

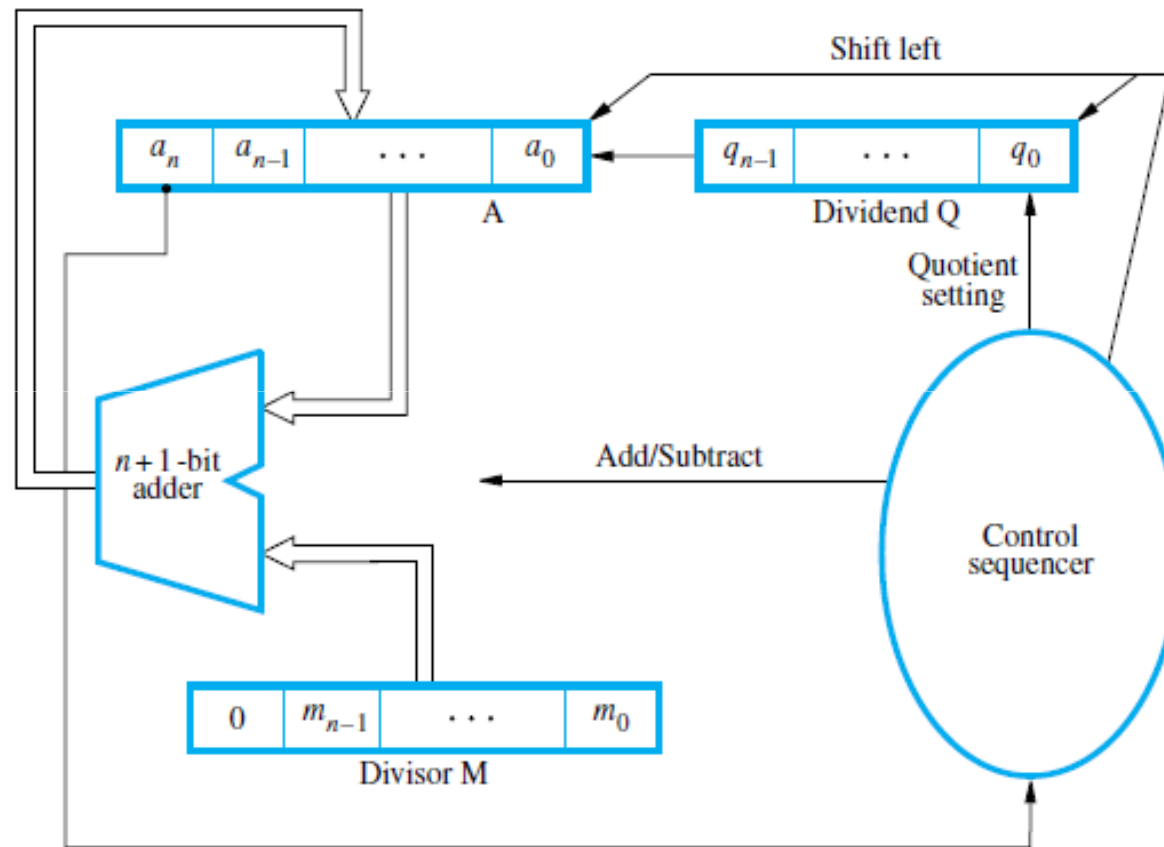

Circuit arrangement for binary division.




# Restoring Division

Do the following three steps  $n$  times:

1. Shift A and Q left one bit position.
2. Subtract M from A, and place the answer back in A.
3. If the sign of A is 1, set  $q_0$  to 0 and add M back to A (that is, restore A); otherwise, set  $q_0$  to 1.
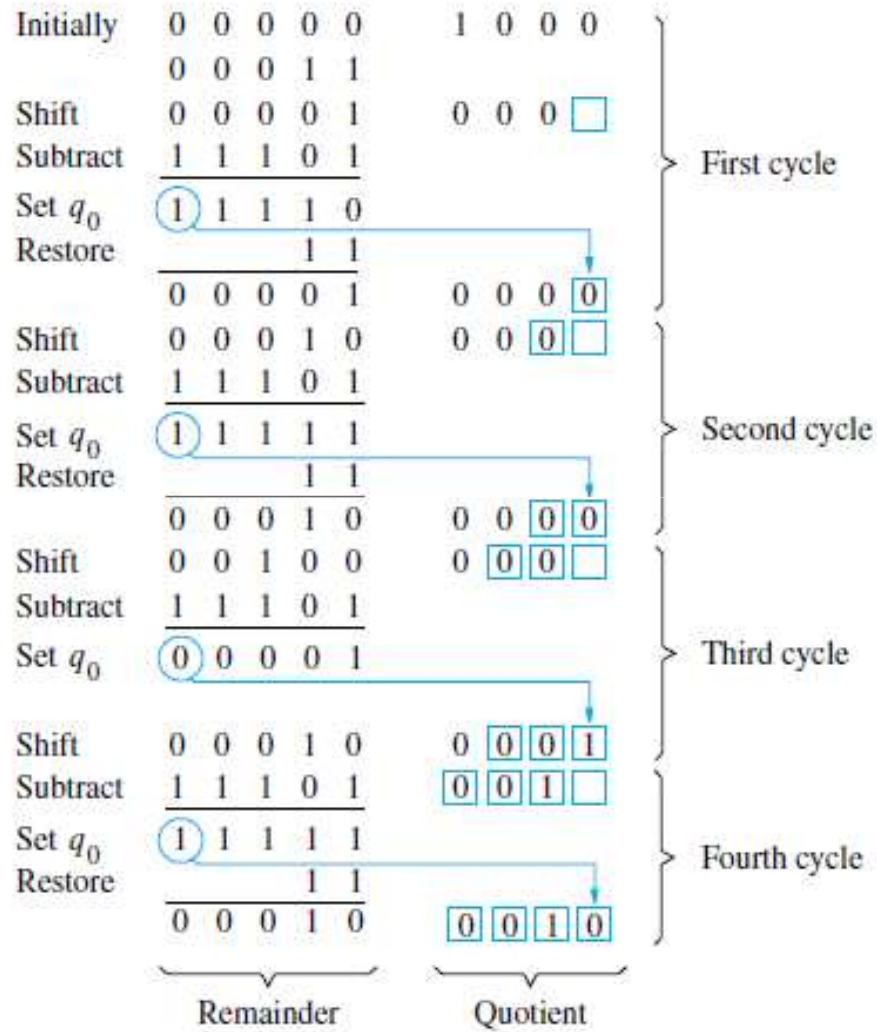
# Restoring Division

$$\begin{array}{r} 10 \\ 11 \overline{) 1000} \\ \underline{11} \phantom{00} \\ 10 \end{array}$$



A restoring division example.


# Non-Restoring Division

Stage 1: Do the following two steps  $n$  times:

1. If the sign of  $A$  is 0, shift  $A$  and  $Q$  left one bit position and subtract  $M$  from  $A$ ; otherwise, shift  $A$  and  $Q$  left and add  $M$  to  $A$ .
2. Now, if the sign of  $A$  is 0, set  $q_0$  to 1; otherwise, set  $q_0$  to 0.

Stage 2: If the sign of  $A$  is 1, add  $M$  to  $A$ .

# Non-Restoring Division

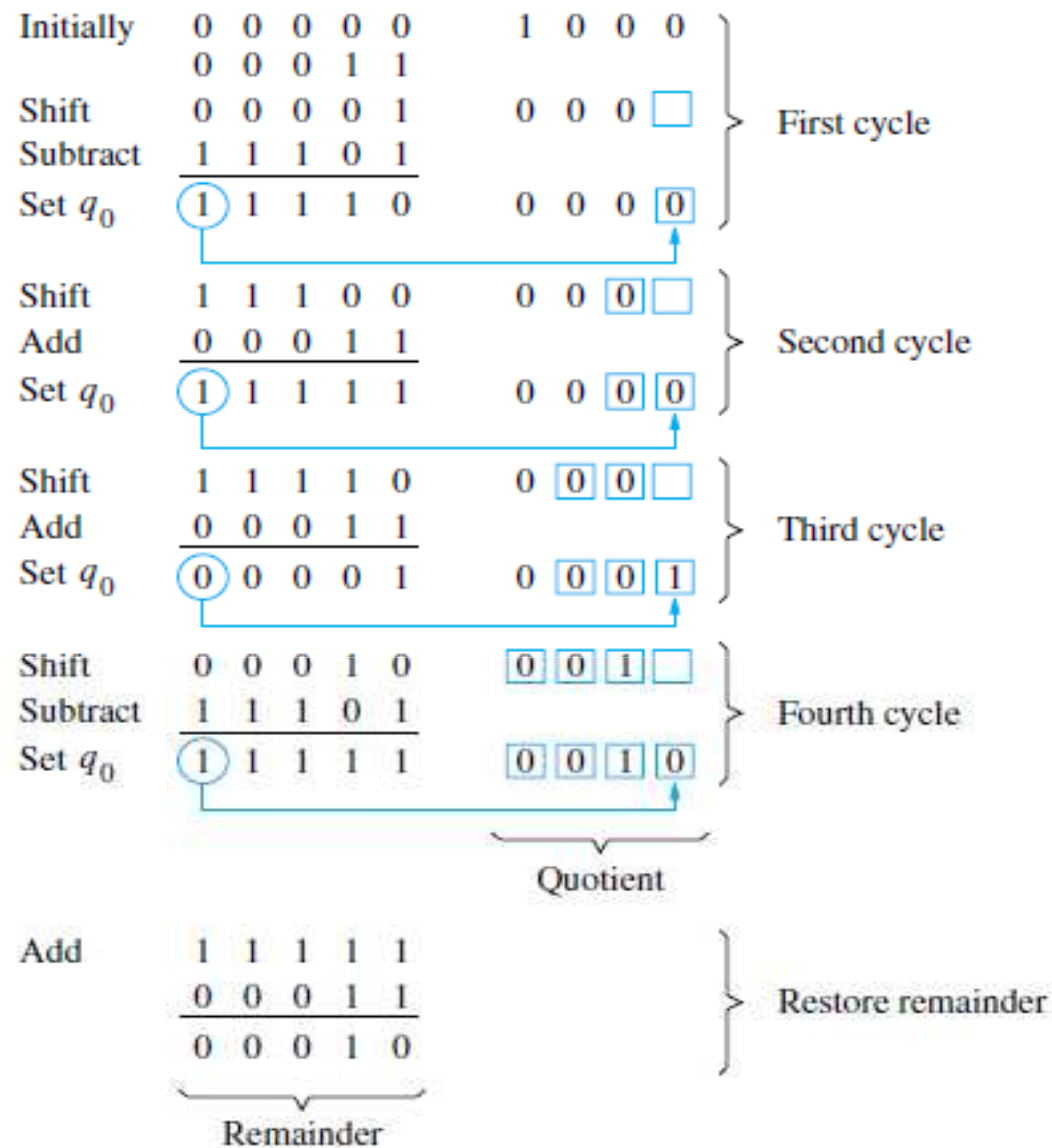

A non-restoring division example.