


BINARY ADDER-SUBTRACTOR

Half Adder

- Circuit needs two binary inputs and two binary outputs

Half Adder

<i>x</i>	<i>y</i>	<i>C</i>	<i>S</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 


(a) $S = xy' + x'y$
 $C = xy$

Half Adder

- Two half adders can be used to construct a full adder
- $S = x'y + xy' = x \oplus y$

$$S = x'y + xy'$$
$$C = xy$$

 

Full Adder

- *Addition of n -bit binary numbers requires the use of a full adder*
- *Addition proceeds on a bit-by-bit basis*
- *Right to left, beginning with the least significant bit*
- *Must consider a possible carry out from the previous position*

Full Adder

- A full adder add three bits and produces two output
- Input variables, denoted by x and y , represent the two significant bits to be added
- The third input, z , represents the carry from the previous lower significant position
- Output bits are Sum and carry

Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = x'y'z + x'yz' + xy'z' + xyz$$

$$C = xy + xz + yz$$


Full Adder

Full Adder


x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = x'y'z + x'yz' + xy'z' + xyz$$

$$C = xy + xz + yz$$

 

(a) $S = x'y'z + x'yz' + xy'z' + xyz$

 


(b) $C = xy + xz + yz$

Full Adder

$$S = x'y'z + x'yz' + xy'z' + xyz$$

$$C = xy + xz + yz$$

 

Full Adder


$$S = x'y'z + x'yz' + xy'z' + xyz$$

$$C = xy + xz + yz$$

$$\begin{aligned} S &= z \oplus (x \oplus y) \\ &= z'(xy' + x'y) + z(xy' + x'y)' \\ &= z'(xy' + x'y) + z(xy + x'y') \\ &= xy'z' + x'yz' + xyz + x'y'z \end{aligned}$$

$$\begin{aligned} C &= z(xy' + x'y) + xy = xy'z + x'yz + xy \\ &\quad (x \oplus y)z + xy \end{aligned}$$

Full Adder

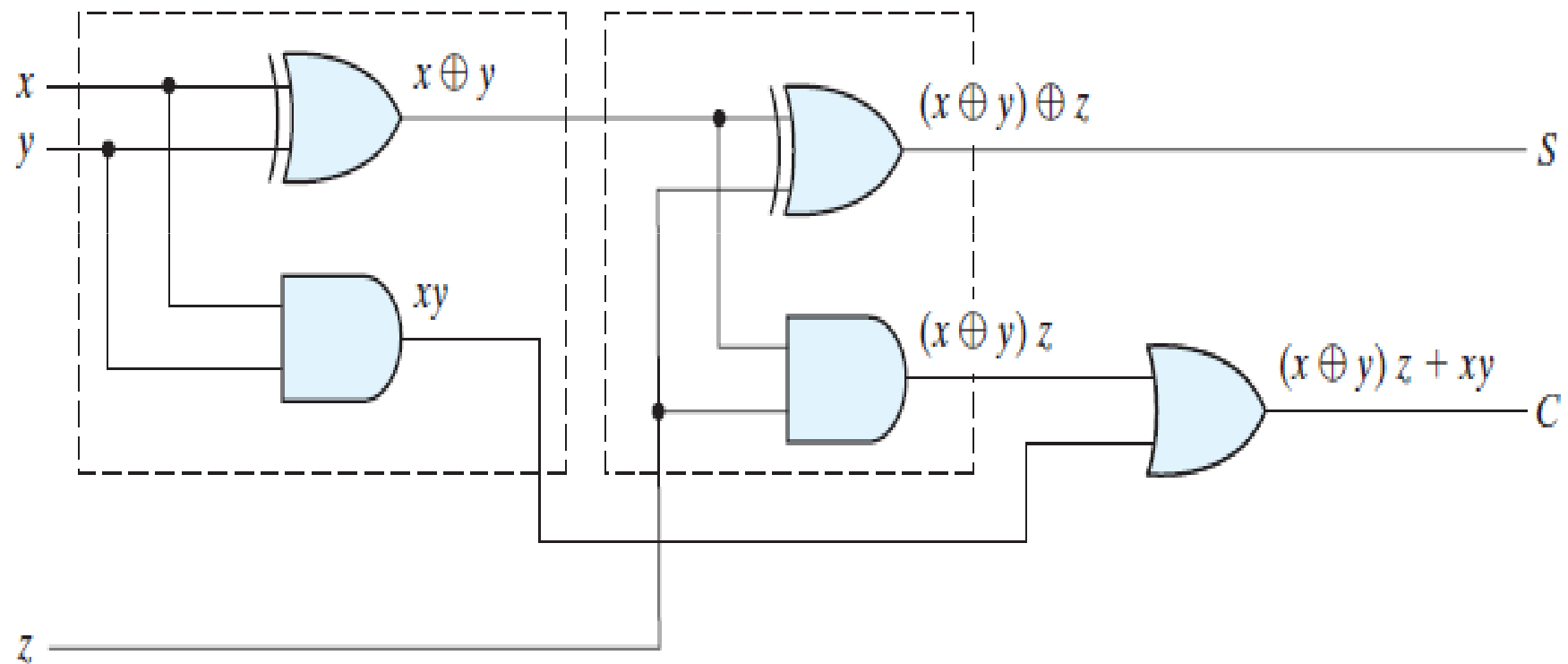

Binary Adder


- Constructed with full adders connected in cascade
- Output carry from each full adder connected to the input carry of the next full adder in the chain
- Addition of *n-bit numbers requires a chain of n full adders*

Binary Adder


Subscript i :	3	2	1	0	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}

Binary Adder


Ripple Carry Adder

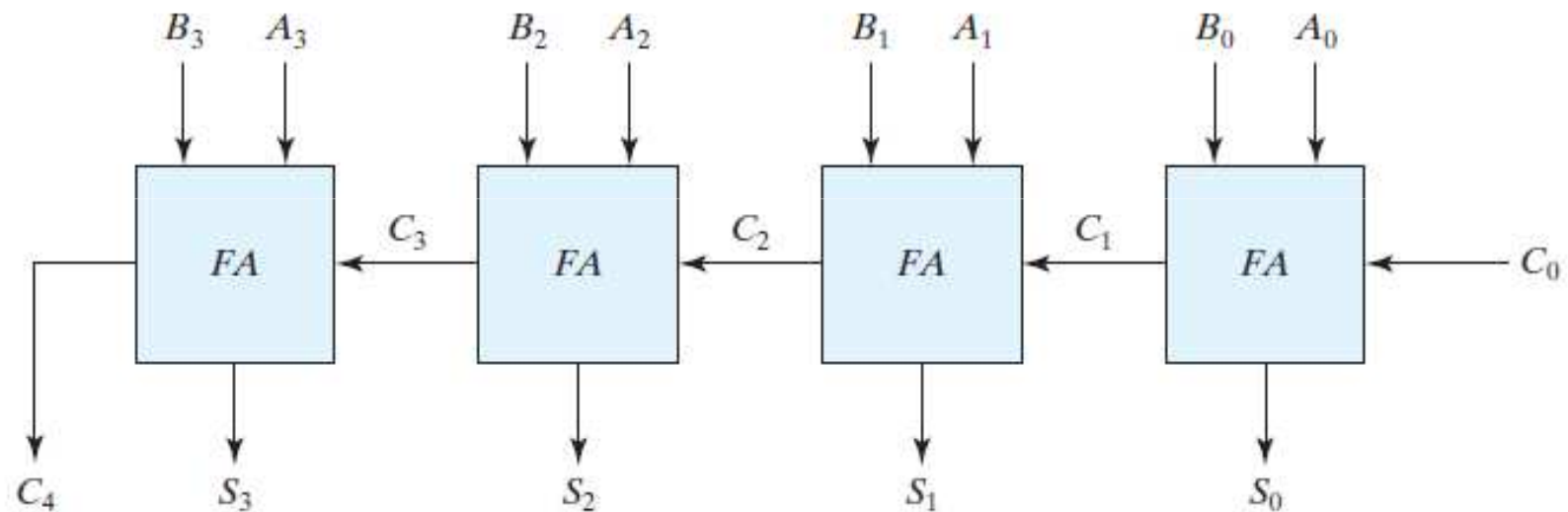

Binary Adder

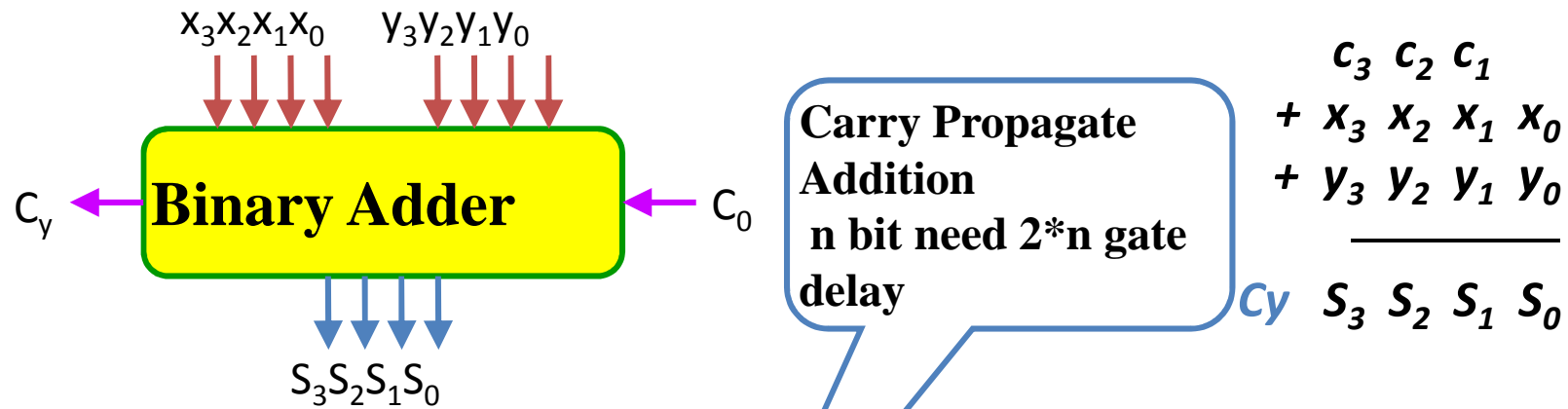

 
$$\begin{array}{r}
 c_3 \ c_2 \ c_1 \\
 + \ x_3 \ x_2 \ x_1 \ x_0 \\
 + \ y_3 \ y_2 \ y_1 \ y_0 \\
 \hline
 c_y \ s_3 \ s_2 \ s_1 \ s_0
 \end{array}$$



Parallel Adders

- Reduce the carry propagation delay
 - Employ faster gates
 - Look-ahead carry (more complex mechanism, yet faster)
 - Carry propagate: $P_i = A_i \oplus B_i$
 - Carry generate: $G_i = A_i B_i$
 - Sum: $S_i = P_i \oplus C_i$
 - Carry: $C_{i+1} = G_i + P_i C_i$
 - $C_0 = \text{Input carry}$
 - $C_1 = G_0 + P_0 C_0$
 - $C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0)$
 - $C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$

 

Carry Propagation

P_i is the carry Propagator


G_i is the carry Generator

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

 

Carry Propagation

- Let's look at the carry out equations for specific bits, using the general equation from the previous page $C_{i+1} = G_i + P_i C_i$.

$$C_1 = G_0 + P_0 C_0$$

$$\begin{aligned} C_2 &= G_1 + P_1 C_1 \\ &= G_1 + P_1 (G_0 + P_0 C_0) \\ &= G_1 + P_1 G_0 + P_1 P_0 C_0 \end{aligned}$$

$$\begin{aligned} C_3 &= G_2 + P_2 C_2 \\ &= G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0) \\ &= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \end{aligned}$$


$$\begin{aligned} C_4 &= G_3 + P_3 C_3 \\ &= G_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0) \\ &= G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0 \end{aligned}$$

Ready to see the circuit?




- These expressions are all sums of products, so we can use them to make a circuit with only a two-level delay.

Carry Lookahead Logic

 


Carry Lookahead adder

 

Binary Adder

- Carry Propagate Adder

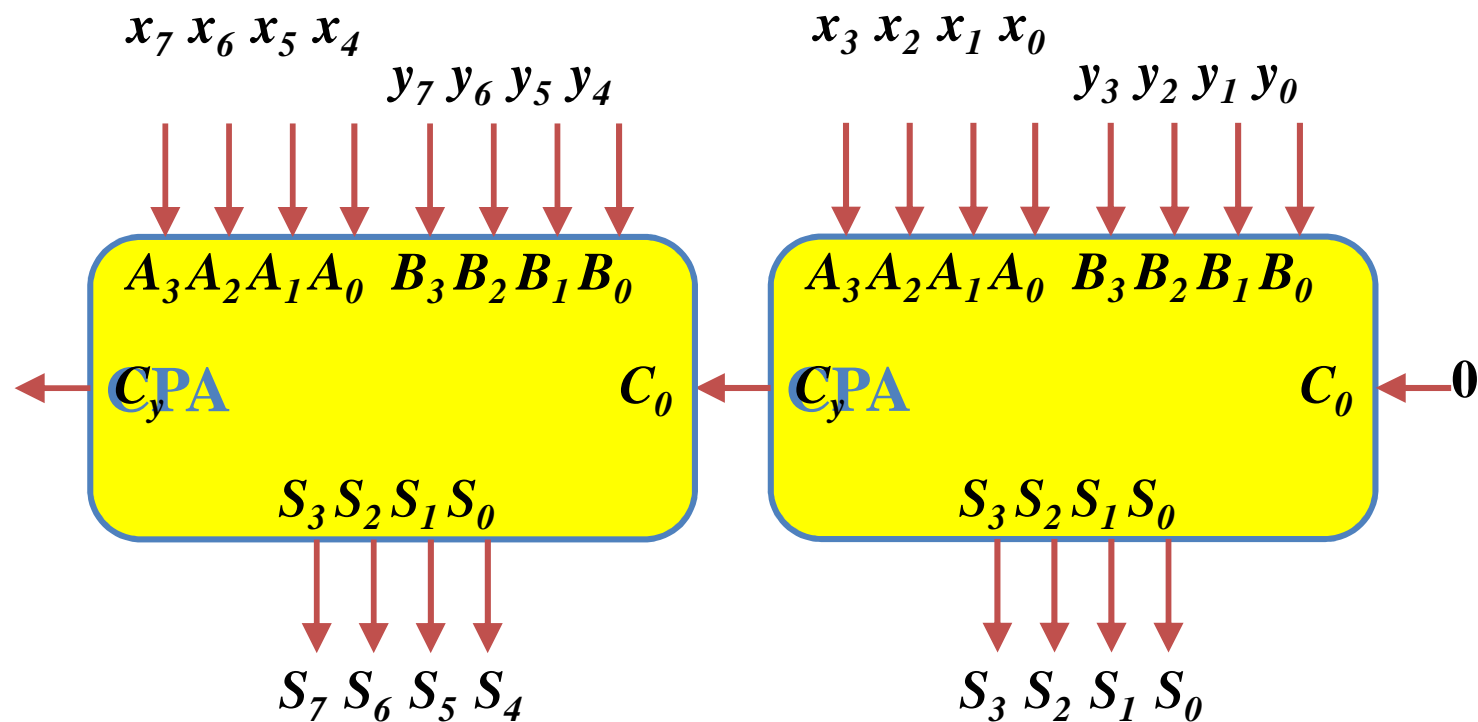


Half Subtractor

Inputs		Outputs	
X	Y	D	B_{out}
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$D = X \oplus Y$$


$$B_{out} = \overline{X} \cdot Y$$

 


Full Subtractor

Inputs			Outputs	
X	Y	B_{in}	D	B_{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

 
$$D = A \oplus B \oplus B_{in} \text{ and } B_{out} = A'B_{in} + A'B + BB_{in}$$



 Making a full subtractor from a full adder



Adder/Subtractor-2

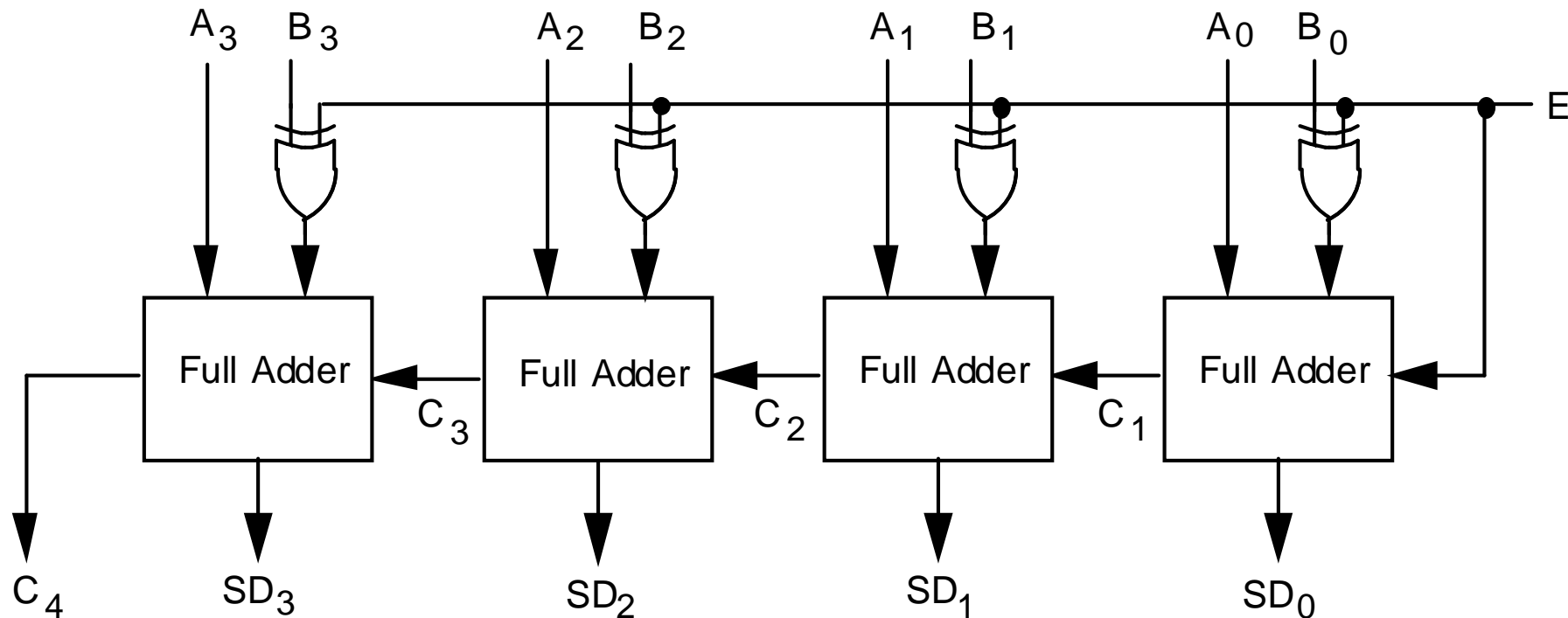


E = 0: 4-bit adder

E = 1: 4-bit subtractor

B	E	B xor E	
0	0	0	E=0 Add
1	0	1	
0	1	1	E=1 Sub
1	1	0	

4-bit Adder: E = 0

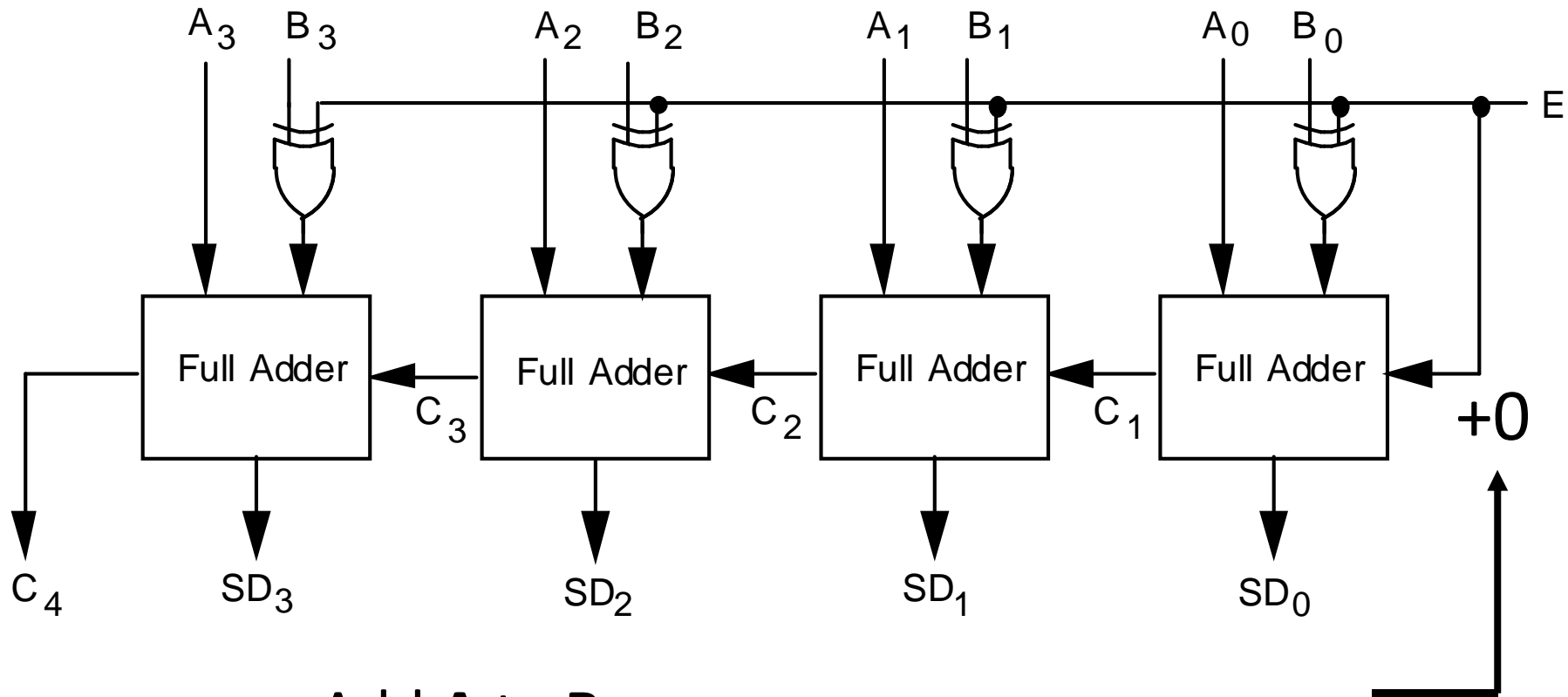


Add **A** to **B**

That is, add **A** to **B**

$$\mathbf{D = A + B}$$

4-bit Subtractor: E = 1

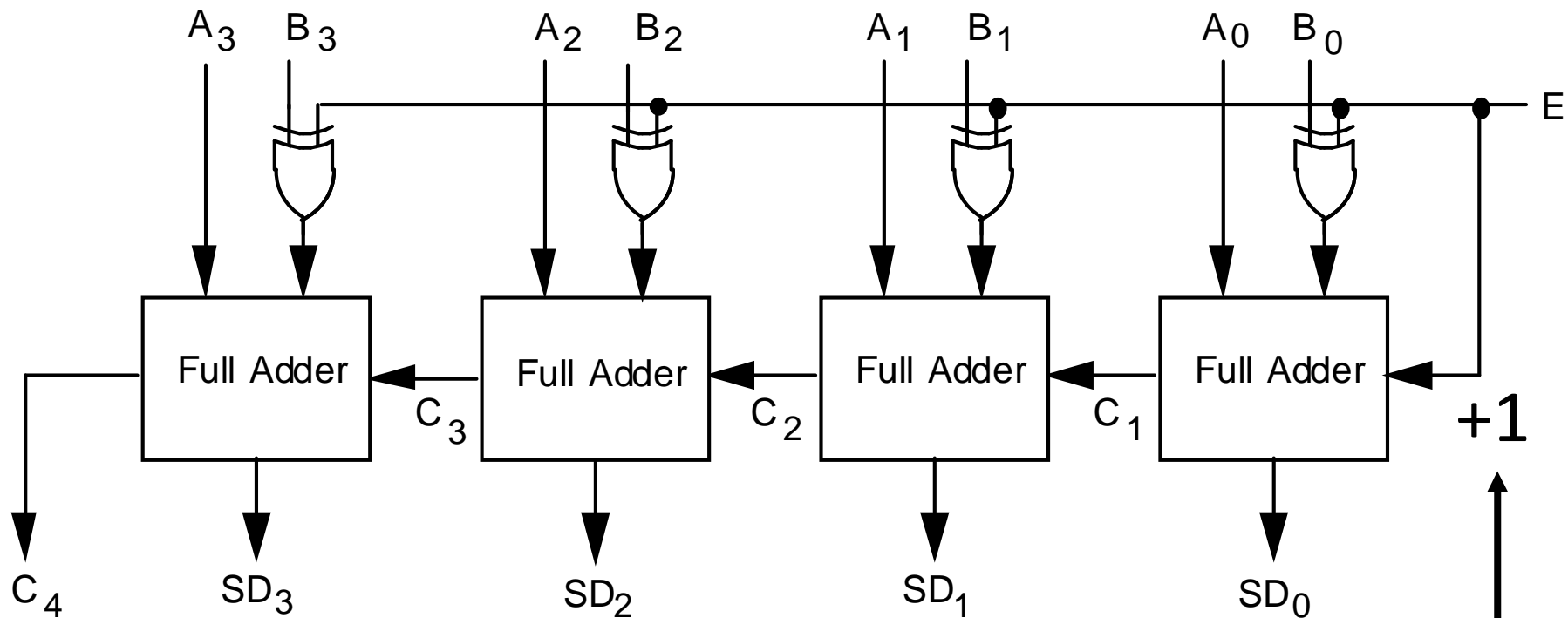

Add **A** to **!B** (one's complement) plus 1
That is, add **A** to two's complement of **B**
D = A - B

Checking Overflow

- V detects overflow
- $V=0$ means no overflow
- $V=1$ means the result is wrong because of overflow
- Overflow - when adding two numbers of the same sign (both negative or positive)
- And result can not be shown with the available bits.

C3	C4	$V = C3 \text{ xor } C4$
0	0	0
1	0	1 overflow
0	1	1 overflow
1	1	0

4-bit adder subtractor with overflow

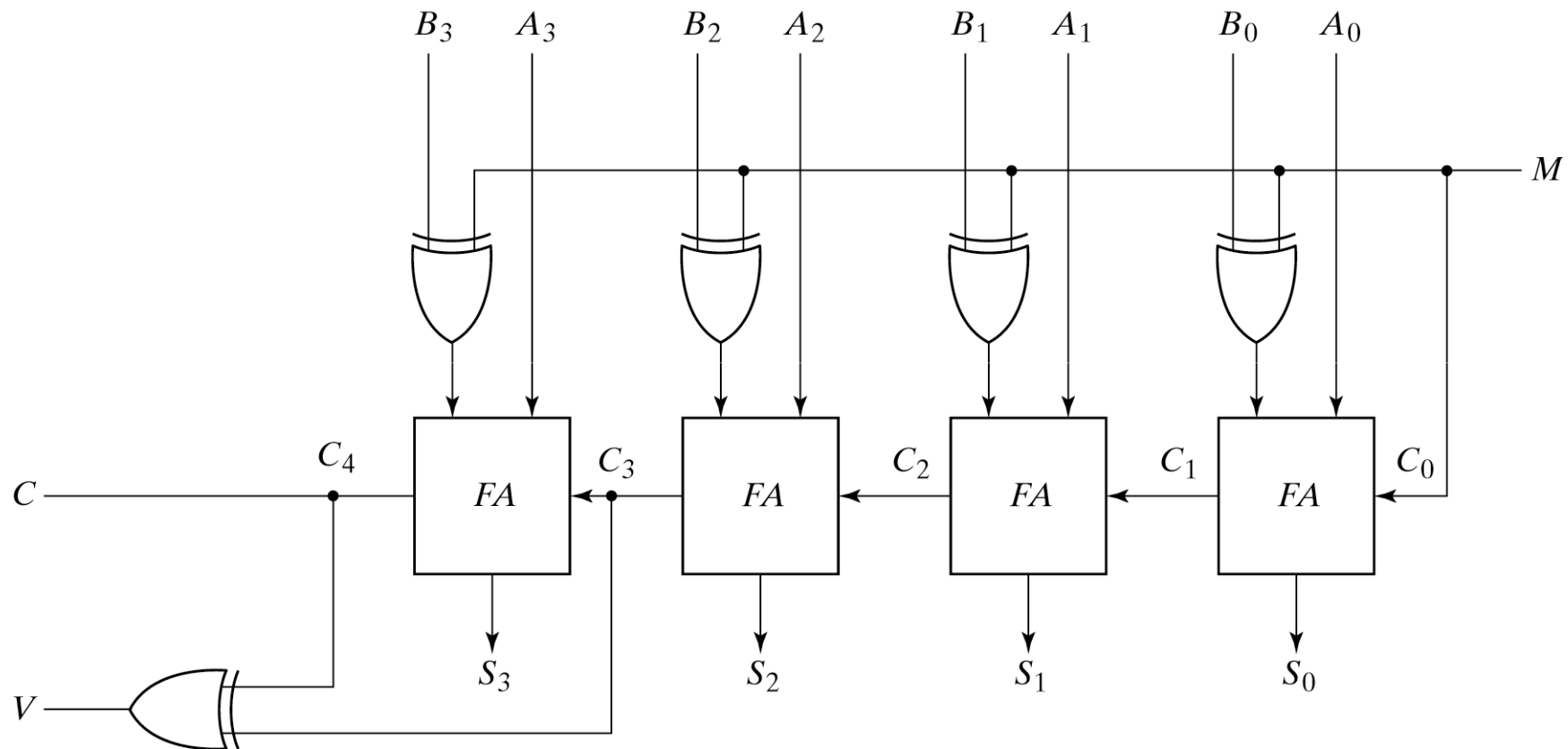


Fig. 4-13 4-Bit Adder Subtractor